



Digital Verilog HDL Project

Name: Nafe Abubaker

ID : 1200047

Section: 5

## Description

Implementing a BCD Adder-Subtractor circuit :

 


Figure 1 BCD adder-subtractor circuit

First we started with the 9's Complementer :

**1) Code :**

First we used the truth table (found at the end of the report), and after minimization we came up with several equations.

1)  $A = w'x'y'$

2)  $B = x'y + xy'$  (Which is XOR)


3)  $C = Y$

4)  $D = z'$

Then used dataflow to implement the found equations and came up with this code:

```
1 module Complement_9(BCDin,BCDout);
2
3
4   input [3:0]BCDin;
5   output [3:0]BCDout;
6
7   //BCDin 3 = a
8   //BCDin 2 = b
9   //BCDin 1 = c
10  //BCDin 0 = d
11  //-----
12  //BCDout 3 = w
13  //BCDout 2 = x
14  //BCDout 1 = y
15  //BCDout 0 = z
16
17  assign BCDout[3] = ((~(BCDin[3])) & (~(BCDin[2])) & (~(BCDin[1])));
18  assign BCDout[2] = BCDin[2] ^ BCDin[1];
19  assign BCDout[1] = BCDin[1];
20  assign BCDout[0] = ~BCDin[0];
21
22 endmodule
```

## 2) Simulation:

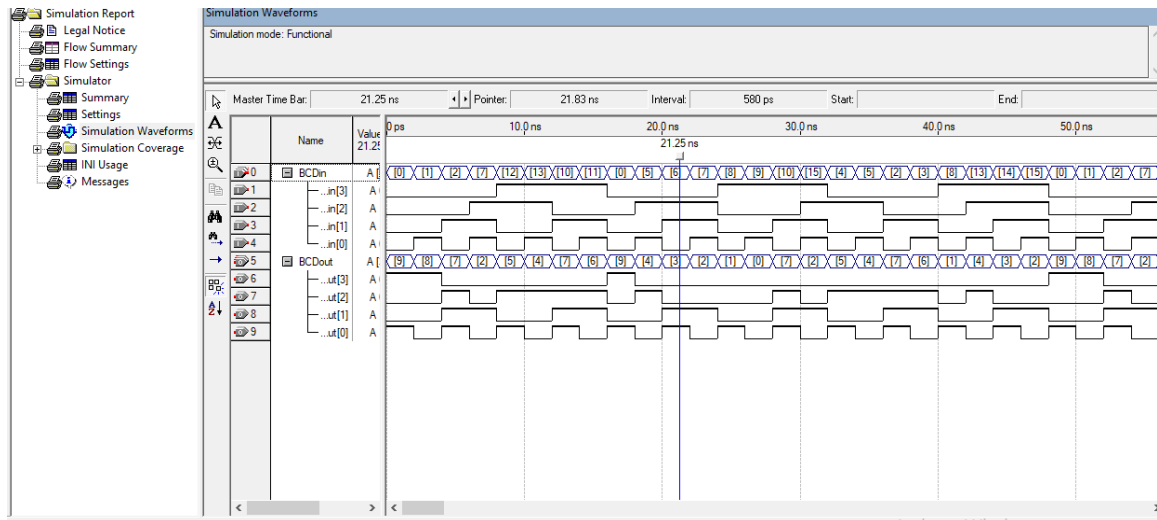

## Quad 2x1 Mux :

We used behavioral to implement 2x1 mux and came up with this code which will set the output to the first 4 bits if the selection equals zero, and will set the output to the

Next 4 bits if the selection equals one.


### 1) Code

```

1  module QuadMux(input [3:0]BCDout,BCDin,input sel,output reg [3:0]out);
2
3  always @(BCDout,BCDin,sel) begin
4      if(sel == 0) out = BCDin;
5
6      else out = BCDout;
7
8      end
9
10 endmodule

```

### 2) Simulation

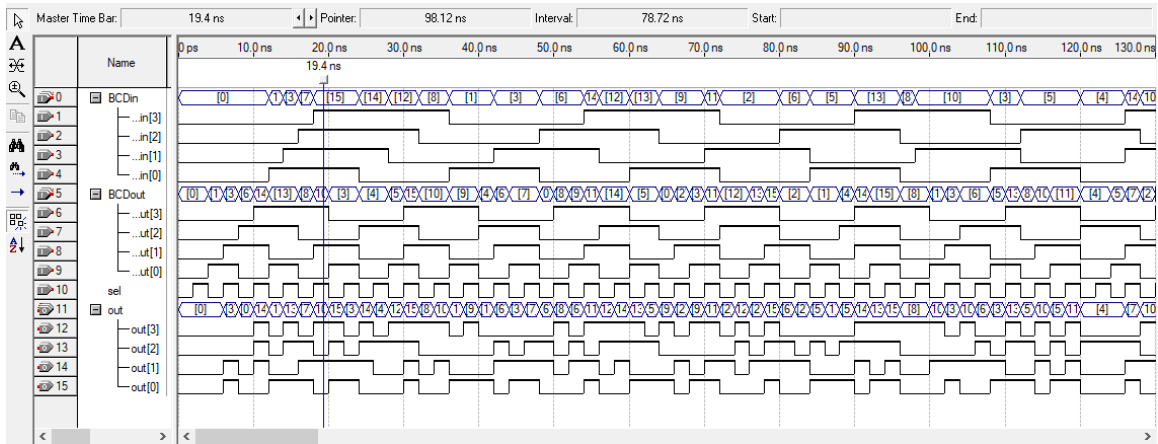

**Last but not least : BCD Adder :**


**We used Full\_Adder(Code is in the end of the report) function to implement the BCD Adder, First 4 bits will be added normally using the full adder, after the addition, We did another addition which will add 6 if the sum of the previous addition is more than 9. And came up with this code.(Using dataflow)**

```

1  module BCD_Adder(input [3:0]Muxoutput,A,input c_in,output [3:0]S);
2
3  wire [3:0] Z,C_out,cout;
4  wire OutputCarry;
5
6
7  Full_Adder F1(Muxoutput[0],A[0],c_in,Z[0],C_out[0]);
8  Full_Adder F2(Muxoutput[1],A[1],C_out[0],Z[1],C_out[1]);
9  Full_Adder F3(Muxoutput[2],A[2],C_out[1],Z[2],C_out[2]);
10 Full_Adder F4(Muxoutput[3],A[3],C_out[2],Z[3],C_out[3]);
11
12 assign OutputCarry = ((C_out[3]) | (Z[3]&Z[2]) | (Z[3]&Z[1]));
13 //if OutputCarry =1 , then it will add 6(4b'0110) to the sum, if not
14 //, the sum will be added to 0(4b'0000) which will remain the same.
15 Full_Adder F5(Z[0],0,0,S[0],cout[0]);
16 Full_Adder F6(Z[1],OutputCarry,cout[0],S[1],cout[1]);
17 Full_Adder F7(Z[2],OutputCarry,cout[1],S[2],cout[2]);
18 Full_Adder F8(Z[3],0,cout[2],S[3],cout[3]);
19
20 endmodule

```


## Simulation:

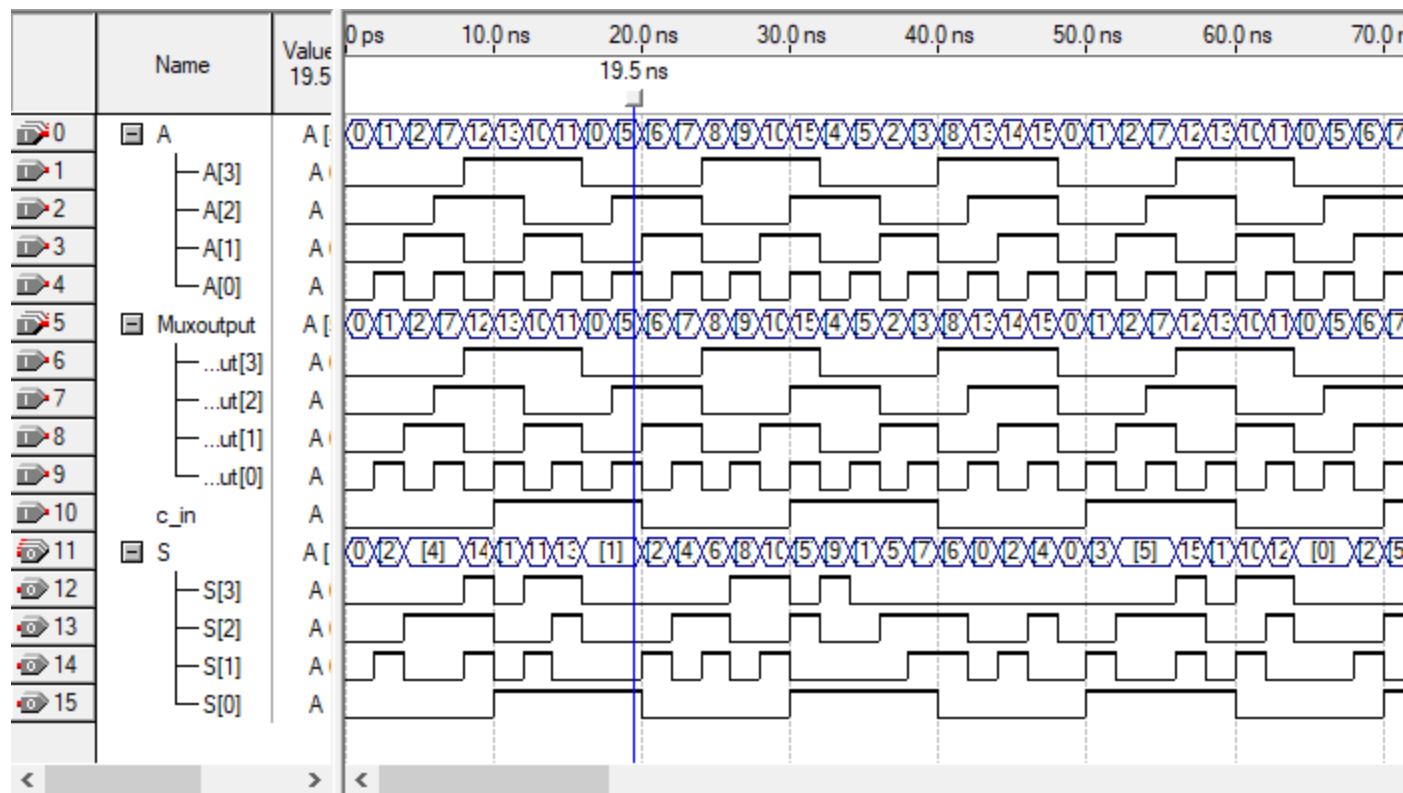

**Finally :**

**The block diagram :**

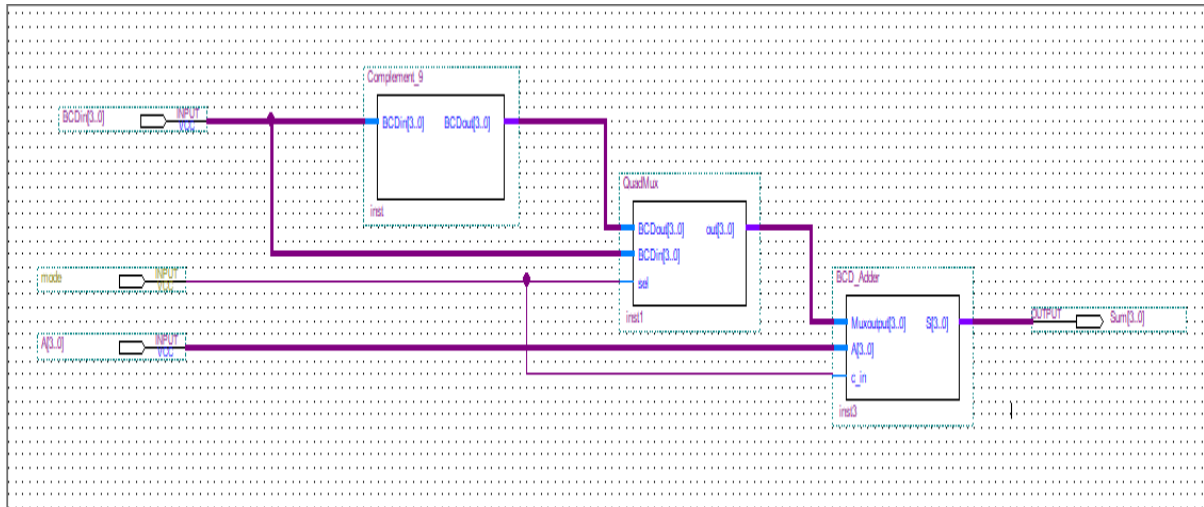**Everything is connected successfully and the result is below.**




```

1  module final_code(input[3:0] BCD_in,A,input mode,output [3:0] S);
2
3  wire[3:0]BCD_out;
4  wire[3:0]out;
5
6  Complement_9 a1(BCD_in,BCD_out);
7  QuadMux a2(BCD_out,BCD_in,mode,out);
8  BCD_Adder a3(out,A,mode,S);
9
10 endmodule

```

## Simulation

 



Truth tables used:

1) 9's Complement

The image shows a handwritten truth table for the 9's Complement operation. It is divided into two parts: BCD and 9's comp.

BCD				9's comp			
W	X	Y	Z	A	B	C	D
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0

2) QuadMux

Select	Inputs		Output
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	1

### 3)BCD Adder


Binary Sum					BCD Sum					Decimal
K	Z <sub>0</sub>	Z <sub>4</sub>	Z <sub>2</sub>	Z <sub>1</sub>	C	S <sub>0</sub>	S <sub>4</sub>	S <sub>2</sub>	S <sub>1</sub>	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
.....										
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

Derivation of BCD adder

Full Adder code:

```
1  module Full_Adder(a,b,C_in,sum,C_out);  
2  
3  input a,b,C_in;  
4  output sum,C_out;  
5  
6  assign C_out = (a&b) | (a&C_in) | (b&C_in);  
7  assign sum = a^b^C_in;  
8  
9  endmodule  
10  
11  █
```

**Full adder- simulation:**

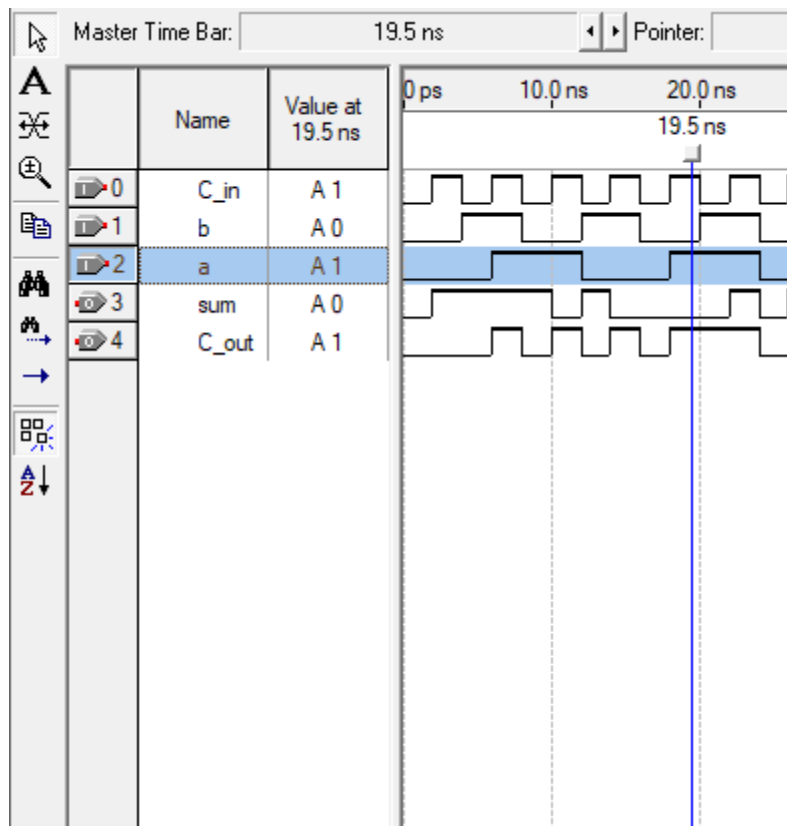

**All Codes used(in writing) :**

**1)9's Complement:**

```
module Complement_9(BCDin,BCDout);
```

```
input [3:0]BCDin;  
output [3:0]BCDout;
```

```
//assign z = ~d;  
//assign y = c;  
//assign x = b^c;  
//assign w = ~a & ~b & ~c;
```

```
//BCDin 3 = a  
//BCDin 2 = b  
//BCDin 1 = c  
//BCDin 0 = d  
//-----  
//BCDout 3 = w  
//BCDout 2 = x  
//BCDout 1 = y  
//BCDout 0 = z
```

```
assign BCDout[3] = ((~(BCDin[3])) & (~(BCDin[2])) & (~(BCDin[1])));
```

```
assign BCDout[2] = BCDin[2] ^ BCDin[1];
```

```
assign BCDout[1] = BCDin[1];
```

```
assign BCDout[0] = ~BCDin[0];
```

```
endmodule
```

---

## 2)MUX

```
module QuadMux(input [3:0]BCDout,BCDin,input sel,output reg [3:0]out);  
  
    always @(BCDout,BCDin,sel) begin  
        if(sel == 0) out = BCDin;  
  
        else out = BCDout;  
  
    end  
  
endmodule
```

---

## 3)Full adder

```
module Full_Adder(a,b,C_in,sum,C_out);  
  
    input a,b,C_in;  
    output sum,C_out;  
  
    assign C_out = (a&b) | (a&C_in) | (b&C_in);
```

```
assign sum = a^b^C_in;
```

```
endmodule
```

---

#### 4)BCD Adder

```
module BCD_Adder(input [3:0]Muxoutput,A,input c_in,output [3:0]S);
```

```
    wire [3:0] Z,C_out,cout;
```

```
    wire OutputCarry;
```

```
        Full_Adder F1(Muxoutput[0],A[0],c_in,Z[0],C_out[0]);
```

```
        Full_Adder F2(Muxoutput[1],A[1],C_out[0],Z[1],C_out[1]);
```

```
        Full_Adder F3(Muxoutput[2],A[2],C_out[1],Z[2],C_out[2]);
```

```
        Full_Adder F4(Muxoutput[3],A[3],C_out[2],Z[3],C_out[3]);
```

```
    assign OutputCarry = ((C_out[3]) | (Z[3]&Z[2]) | (Z[3]&Z[1]));
```

```
    //if OutputCarry =1 , then it will add 6(4b'0110) to the sum, if not, the  
    sum will be added to 0(4b'0000) which will remain the same.
```

```
        Full_Adder F5(Z[0],0,0,S[0],cout[0]);
```

```
        Full_Adder F6(Z[1],OutputCarry,cout[0],S[1],cout[1]);
```

```
        Full_Adder F7(Z[2],OutputCarry,cout[1],S[2],cout[2]);
```

```
        Full_Adder F8(Z[3],0,cout[2],S[3],cout[3]);
```

**endmodule**

---

### **5)Final code**

```
module final_code(input[3:0] BCD_in,A,input mode,output [3:0] S);
```

```
    wire[3:0]BCD_out;
```

```
    wire[3:0]out;
```

```
        Complement_9 a1(BCD_in,BCD_out);
```

```
        QuadMux a2(BCD_out,BCD_in,mode,out);
```

```
        BCD_Adder a3(out,A,mode,S);
```

```
endmodule
```

---

**Done.**



